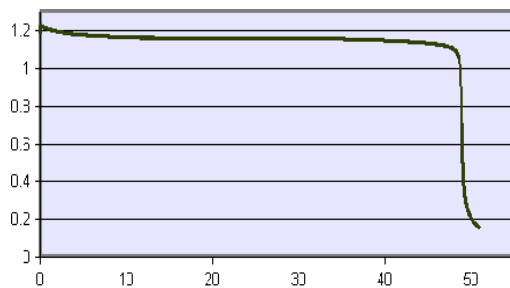


Battery Capacity Characterisation Analyser & Software

Measured discharge characteristic of a 1.2v, 800mAh AA NiCd battery



Measured discharge characteristic of a 12v, 7Ah Lead Acid battery

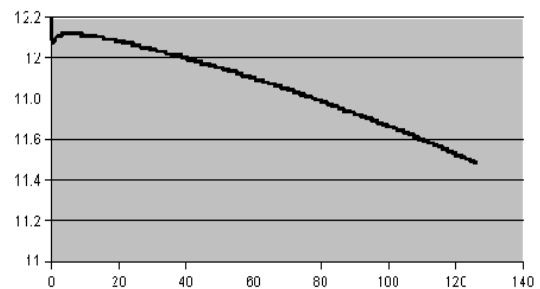


Table of Contents

Introduction.....	2
Basic Circuit Block Diagram.....	3
Three Voltage Power Supply.....	3
+12V Supply ripple under full load with relay coil energised.....	4
Load Control Circuit.....	4
Voltage Amplifier.....	6
Relay Control Circuit (Load Switch).....	7
Voltage Reducer Circuit.....	8
Complete Circuit Diagram, excluding PSU.....	9
Stripboard Layout.....	10
Constructed unit showing PSU board and interface board mounted in box.....	10
Test Load Box.....	11
Calibration.....	12
Interfacing with the Parallel Port.....	13
Software Screenshot.....	14
Visual Basic Project.....	15
Program Modules.....	15
sensors.frm Program Modules.....	17

Introduction

This project is to enable the discharge curves and Capacity of various batteries to be measured.

A battery under test is discharged through a load, which will vary depending on the type of battery being analysed. The voltage of the battery and current delivered through the load are monitored by a computer until the battery voltage falls to the minimum discharge level. The software will then display the capacity of the battery. The unit is controlled via the Parallel port of a PC using Visual Basic 6.

The main components of the circuit are:

Power Supply

This converts the 240V AC mains input to +12V, -12V and +5v.

MAX187 12bit Serial A to D Converter and MAX DG508A Multiplexer

Takes inputs from the Voltage Amplifier (Load Current) and Voltage Reducer (Battery Voltage) circuit via the Multiplexer.

Relay Control Circuit

Switches the Load on or off using a 12V relay.

Voltage Amplifier

Amplifies the Shunt voltage measured across a 0.1ohm resistor in series with the load to bring it within the range of the A to D converter


Voltage Reducer Circuit

Reduces the battery voltage to bring it within the range of the A to D converter

Load

A range of loads will be used depending on the battery type under test.


Basic Circuit Block Diagram

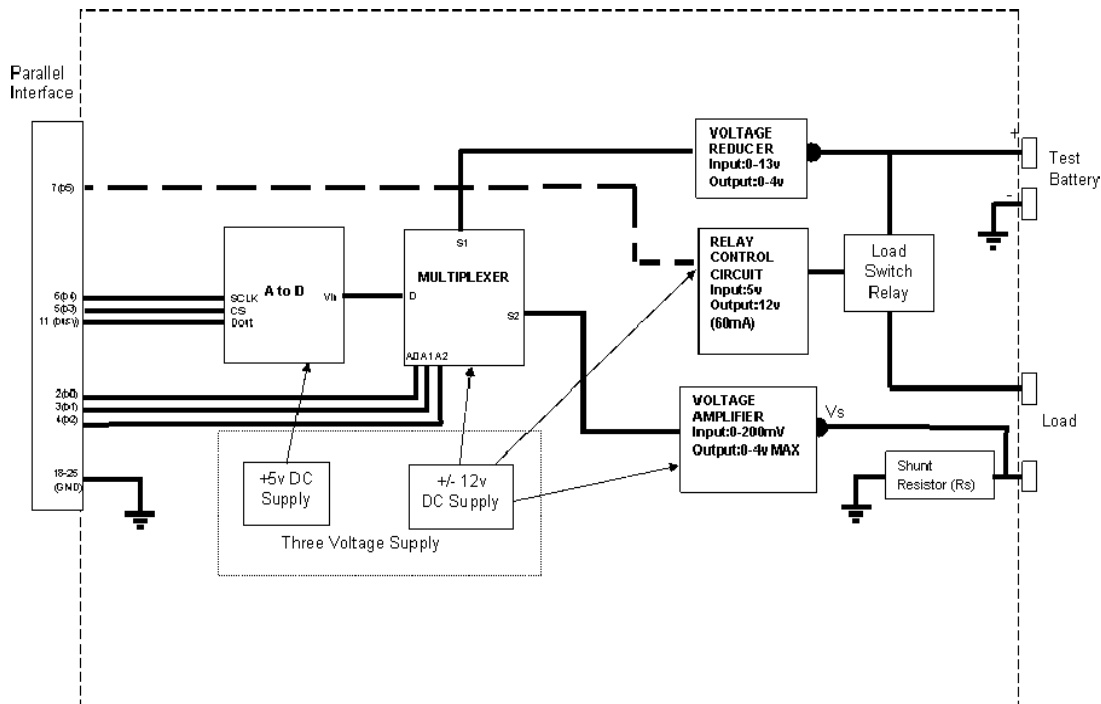


Three Voltage Power Supply

This circuit provides a +/- 12V and a +5V supply.

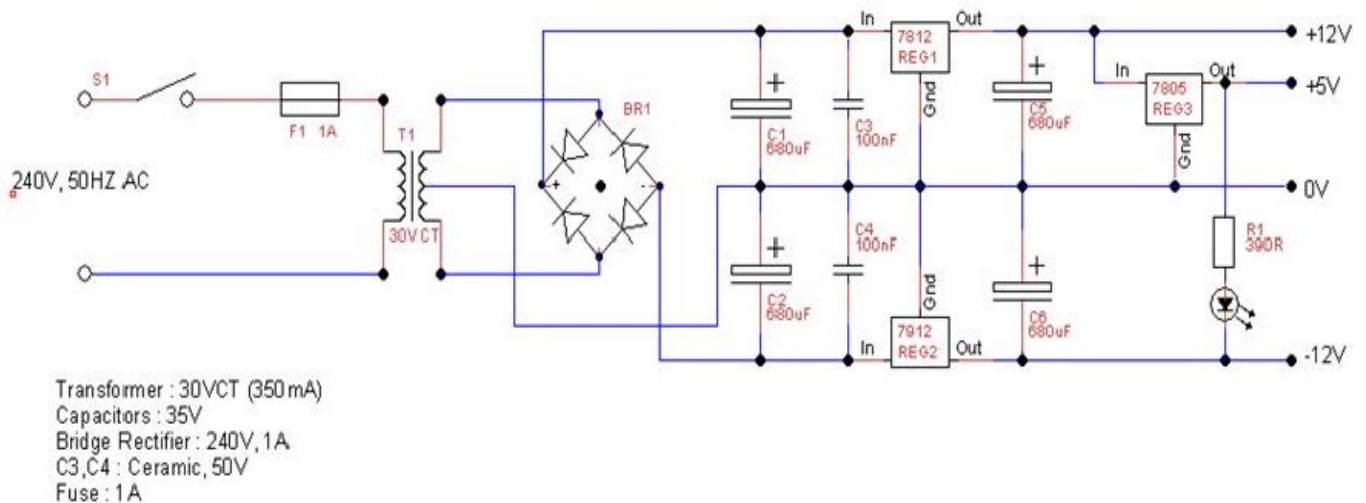- +12V: Relay Coil
- Voltage Amplifier (741 op-amp)
- Multiplexer (MAX DG508A)
- 12V: Voltage Amplifier (741 op-amp)
- Multiplexer (MAX DG508A)
- +5V: AtoD converter (MAX187)



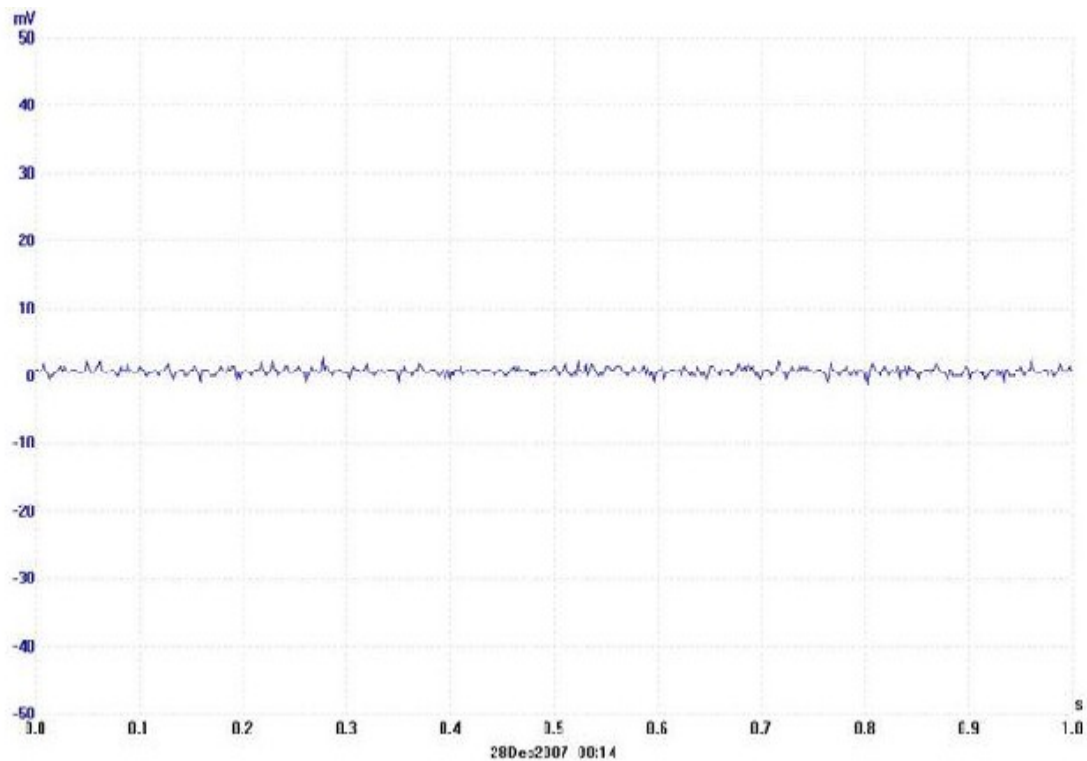+12V Supply ripple under full load with relay coil energised



Load Control Circuit

This circuit consists of the following:

Test Battery


For the circuit shown below, this would typically be any Lead Acid battery with a rating of >1Ah. With different loads, it will be possible to test other batteries.

Load (RL).

This is provided by a load box providing a number of different loads depending on the battery being tested.

Shunt Resistor (Rs)

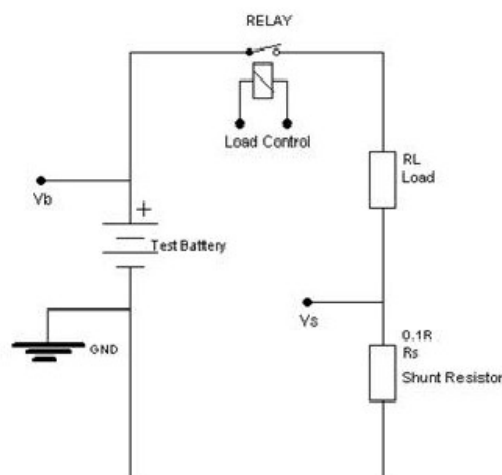This enables the circuit current to be measured. This is a Bare Element Resistor, chosen for its excellent Temperature Coefficient. The circuit current is equal to : $I = V_s / R_s$. In practice I will measure the circuit current using a DMM at different levels and convert the measured voltage into a current reading using software.



Relay

The switching of this relay will be computer controlled; therefore the computer can remove the load when the battery voltage drops below a certain value.

V_b = Battery Voltage.

V_s = Shunt Voltage (Proportional to Circuit Current)

The Load is controlled via the Relay.

EG. 12v, Test Battery

6R Load

Nominal Circuit Current $I = V_b / (R_L + R_s)$

$I = 12 / 6.1 = 2A$ (24W)

The voltage developed across R_s should be : $V = I * R$

$V = 2 * 0.1 = 0.2V$ (200mV)

The computer closes the relay to start the discharge cycle. In practise we won't allow the battery to discharge below a certain value.



Test set-up of circuit diagram

The DMM was used to measure Shunt Voltage (V_s).

With a 12V (1.3Ah) battery the Shunt voltage was 0.160V.

The load current measured with the DMM was 1.500A.

We can now calculate the value of the Shunt Resistor.

$R_s = V_s / I$

$R_s = 0.160 / 1.5 = 0.107\text{ohms}$.

The nominal value of the resistor is 0.1ohms.



In reality the correlation between V_s and the load current should be checked at different current and voltage levels, as it will vary due to the temperature co-efficient of the shunt resistor (20ppm/°C)

In practice, I measured the value of R_s (as above) at up to 12V, 2A load and found its value to change by no more than 10%.

I

Voltage Amplifier

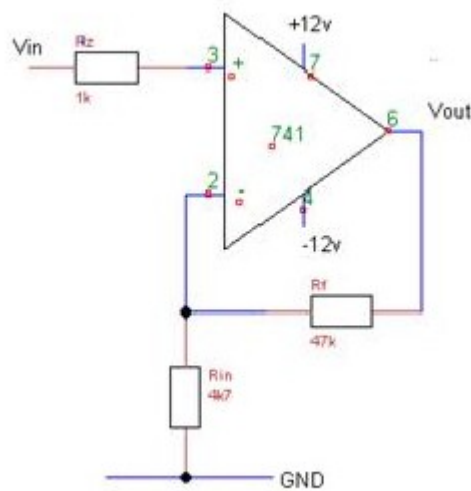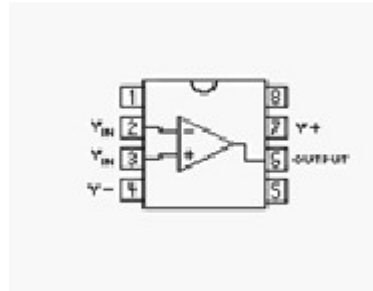The voltage measured across the shunt resistor will vary from approximately 0v to 200mV depending on the load used. The MAX187 AtoD has an input voltage range of 0 to 4v. The non-inverting amplifier below has a gain of 11, which will give a maximum output voltage of $200\text{mV} * 11 = 2.2\text{v}$.



Calculation of Gain

$$\text{Gain} = (R_f + R_{in}) / R_{in}$$

$$\text{Gain} = (47000 + 4700) / 4700 = 11$$

The amplifier was constructed on breadboard and tested as follow:


Input Voltage	Output Voltage	Gain
50.0mV	0.568V	11.4
123mV	1.362V	11

So, the measured gain of the 741 is approximately 11, as caclulated.

Relay Control Circuit (Load Switch)

The relay is triggered by the output of b5 of the parallel port. The relay coil requires 12v to energise. The resistance of the coil is 200ohms, therefore a current of $12\text{v} / 200\text{ohms} = 60\text{mA}$ will be drawn. The parallel port output of 5v at a maximum of 12mA isn't sufficient to energise the relay coil. The circuit below will allow the +5v signal from the parallel port to switch +12v.

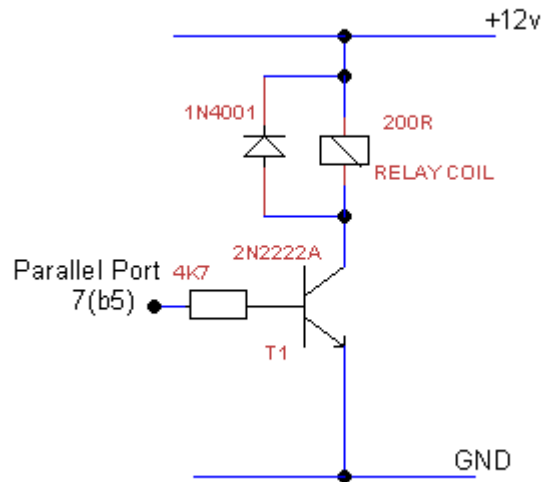The diode protects the transistor from back EMF which will be generated when the relay coil is switched off.



Relay Coil Load Current (I_c) = $12\text{v} / 200\text{R} = 60\text{mA}$

Load Current / Max parallel port current
= $60 / 12 = 5$.

We need a transistor with an $h_{fe} > 5$. It's good practise to choose a transistor h_{fe} of 5x this value i.e 25.


2N2222A chosen – $h_{fe}=100$, $I_{C(\text{max})}=800\text{mA}$

Calculated value for base resistor:

$$R_b = (V_c \cdot h_{fe}) / (5 \cdot I_c)$$


$$R_b = (12 \cdot 100) / (5 \cdot 0.060) = 4000$$

$R_b = 4\text{k}7$ chosen.

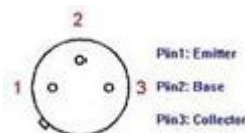

Voltage Reducer Circuit

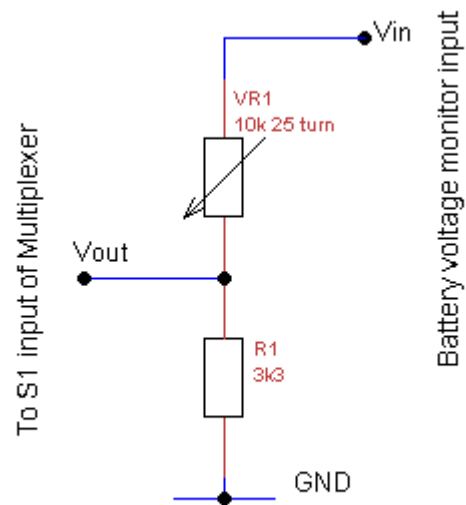The AtoD converter can only accept voltage inputs of up to +4v. As the max voltage of a battery could be >13.5V the voltage needs to be scaled down. A simple potential divider can be used to achieve this.




$$V_{out} = (R1 / (R1 + VR1)) \cdot V_{in}.$$

V_{in} is measured from the positive terminal of the battery under test.


A test voltage of 13.5V was be inputted and VR1 adjusted to give make V_{out} 4v.

Complete Circuit Diagram, excluding PSU.

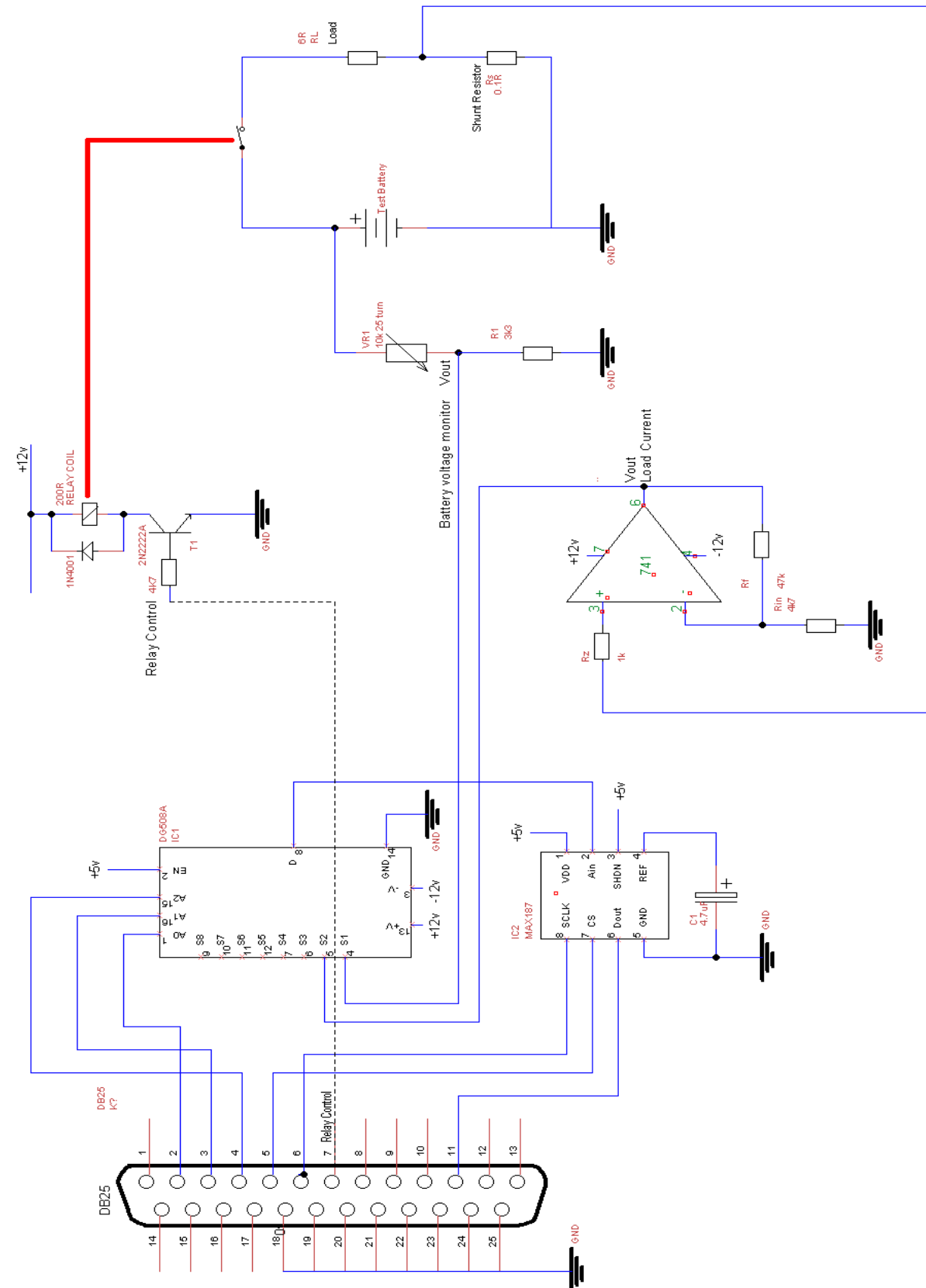


The Battery Voltage from the Voltage Reducer circuit and the Load Current from the Voltage Amplifier are connected to the S1 & S2 inputs of the multiplexer respectively. Address lines A0 to A3 on the multiplexer are used to select the desired input (S1 or S2). The multiplexer can take up to 8 inputs, but for this project I am only using two.

Stripboard Layout

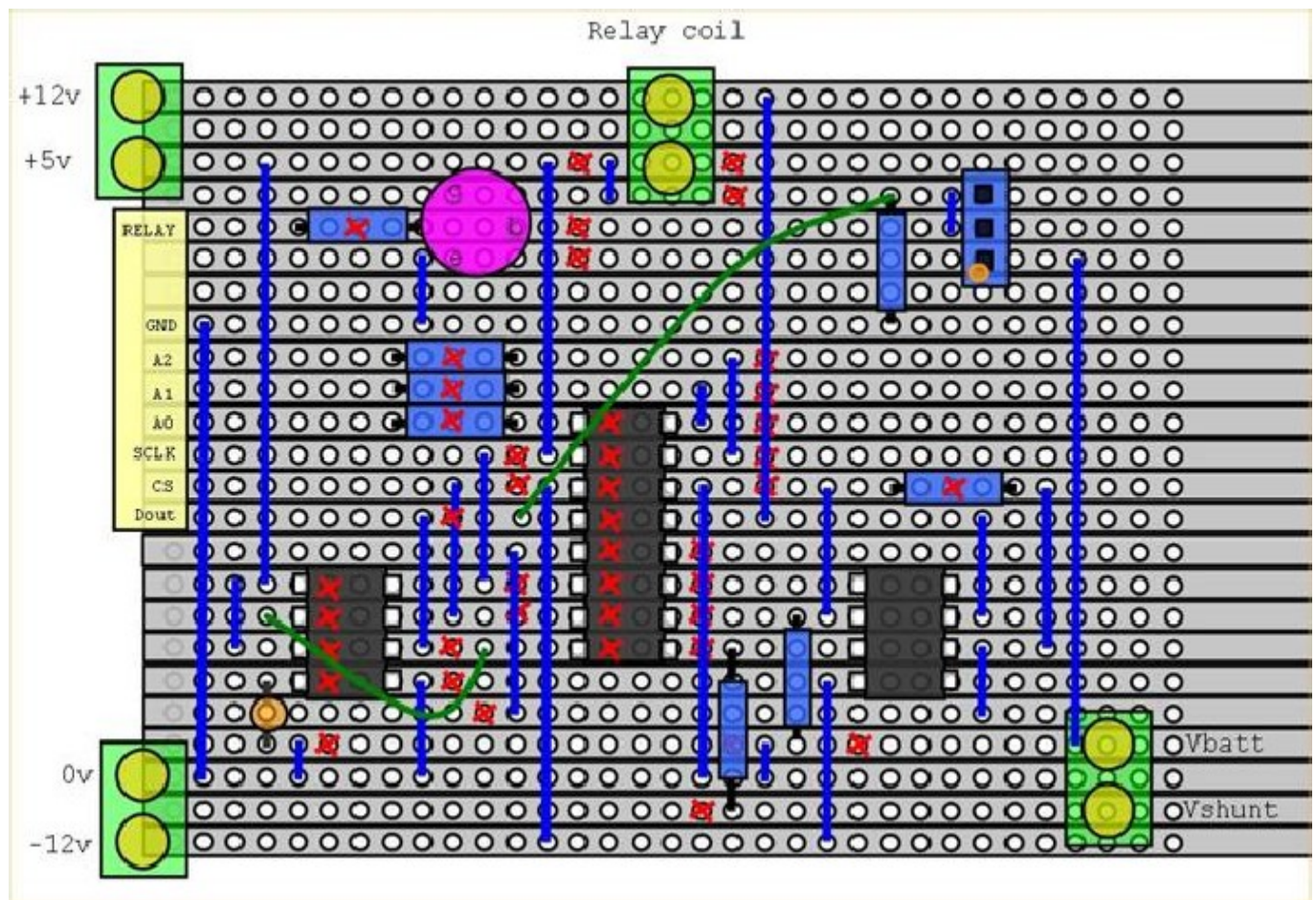

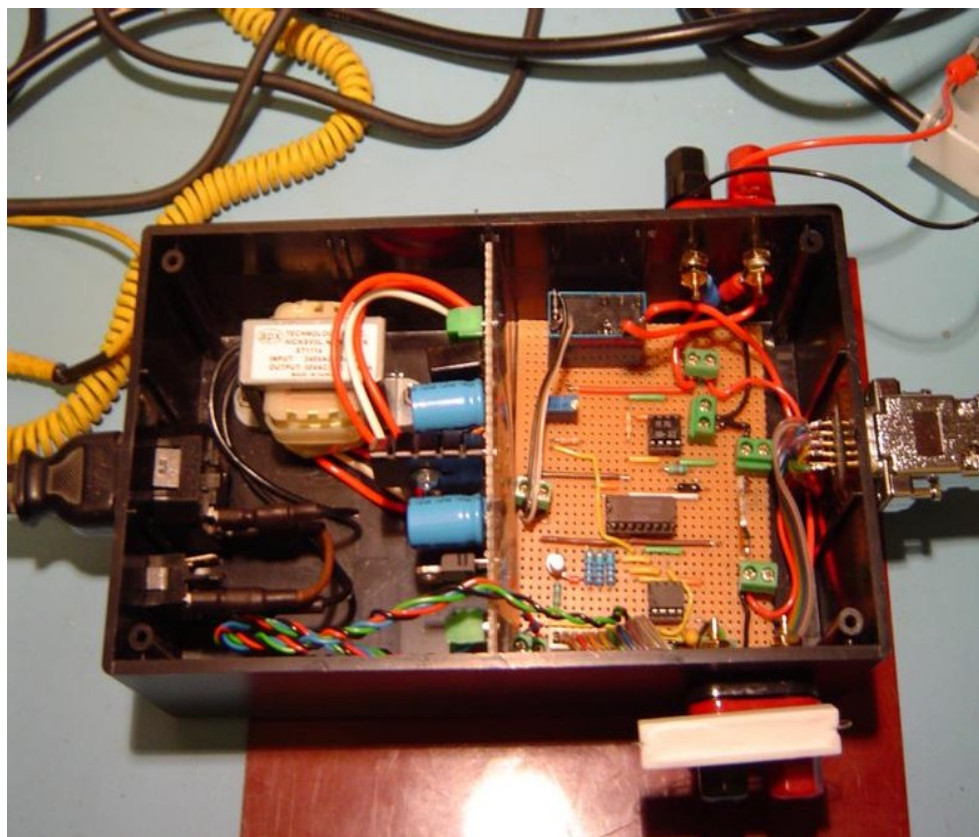Constructed unit showing PSU board and interface board mounted in box




Test Load Box


The test loads are housed within an aluminium casing. Each load is brought outside the box using banana terminals. The test box contains the following loads:


Load	Suitable Use
2 x 15R (50W) Resistors in Parallel = 7R5	6V & 12V batteries at about 1.7 Amps
1.2R (10W) (Plus 0.1R shunt resistor)	1.2 - 1.5V lower capacity batteries Typical discharge current is 1 Amp.
0.22R (25W) (Plus 0.1R shunt resistor)	0.22R (25W) (Plus 0.1R shunt resistor)
47R (25W)	9V batteries. Typical discharge current is 0.2 Amps.

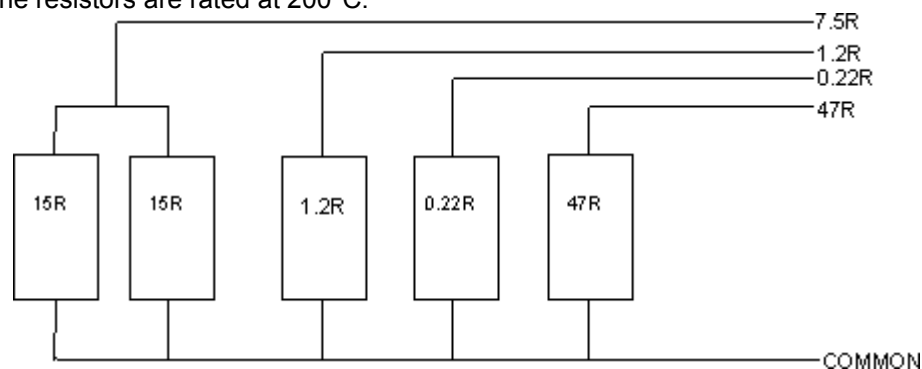Note. If used as above, heat dissipation won't be a problem. Only the two 15R resistors in parallel will get hot. With a fully charged 12V battery, the maximum temperature of the resistors was measured to be 60°C. By placing a 12V fan across the two resistors, and drilling ventilation holes around the resistors, the temperature dropped to less than 50°C. The resistors are rated at 200°C.



Basic Circuit Diagram of Load Box

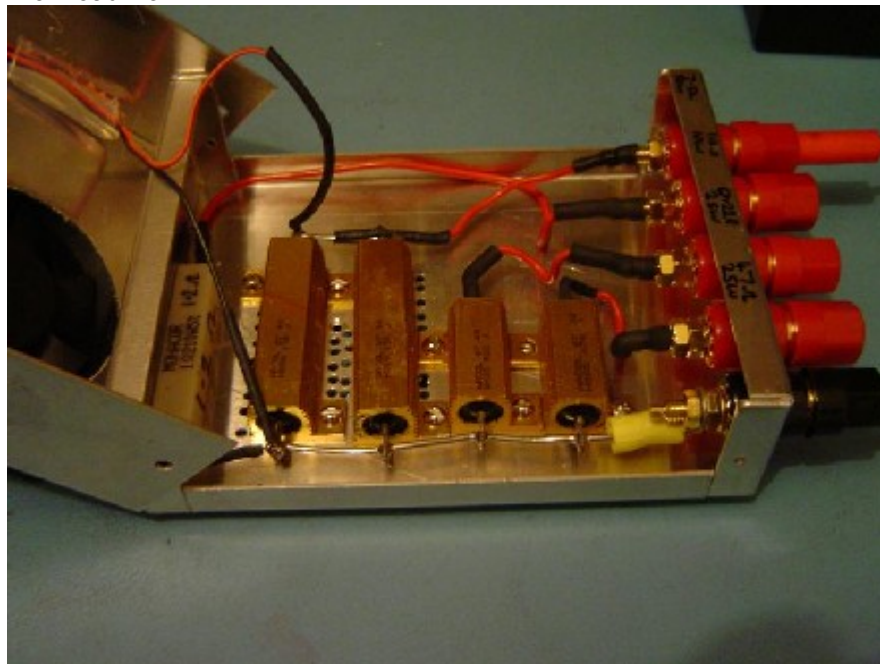

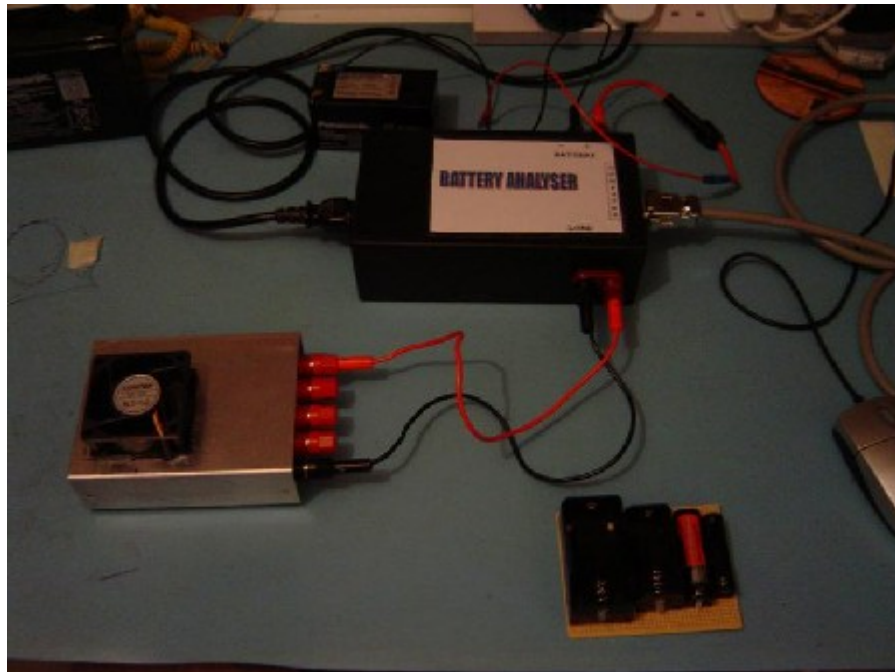

Calibration

The analyser was powered up with a 12v, 20W lamp as a load and a 12V, 1300mAh Lead Acid battery.

Voltage Calibration

The analyser was set to measure battery voltage and the output of the AtoD converter recorded. The AtoD converter output will be a value between 0 and 4096 (12 bit AtoD). To calibrate the output, we need to measure the actual battery voltage using a DMM.

AtoD Output	Actual Battery Voltage
3620	12.17V

If we now divide the AtoD Output by the battery voltage we get a calibration factor of : $3620 / 12.17 = 297.5$
For the software to display the actual battery voltage all it needs to do is divide the AtoD output by the calibration factor.

Current Calibration

The analyser was set to measure current and as above, the AtoD converter output recorded. The actual current was measured using a DMM in series with the battery and load.

AtoD Output	Actual Battery Current
1860	1546mA

If we now divide the AtoD Output by the current we get a calibration factor of : $1860 / 1546 = 1.203$
For the software to display the actual current all it needs to do is divide the AtoD output by the calibration factor.

Measurement of Cal Factor at lower level of Load current

A 1.2V, 2600mAh NiMi battery was used with the 12V, 20W lamp.

<<<Voltage>>>

AtoD Output	Actual Battery Voltage	Cal Factor
327	1.140	286.8

<<<Current>>>

AtoD Output	Actual Battery Current	Cal Factor
636	523mA	1.216

Analyser Linearity

Now that the Cal Factor has been calculated at two different levels, we can work out the linearity of the analyser.

At 12V the cal factor is 297.5. At 1.2V the cal factor is 286.8. The percentage difference between the two cal factors is: 3.6%. So, the analyser can measure the battery voltage with a linearity of at least 3.6% between 1.2V and 12V

Likewise, for Current:

Cal factor at 523mA = 1.216

Cal Factor at 1546mA = 1.203

Linearity between 523mA and 1546mA = 0.25%

NOTE : This circuit is only suitable for analysing batteries up to a maximum of 14V. By up-rating the relay there should be no problems with using higher voltage batteries and higher current loads, although the shunt resistor may also have to be up-rated or mounted on a heat sink.

Interfacing with the Parallel Port

The Data Register and the Status Register of the parallel port are used to interface with the analyser. This can be implemented fairly easily using Visual Basic 6 or MS QuickBasic.

Data Register - Parallel Port Output/Input Lines

Parallel Port Data Register	b0	b1	b2	b3	b4	b5	b6	b7
Circuit Board Connection	A0	A1	A2	CS	SCLK	RELAY CONTROL	NC	NC
Description	DG508A Multiplexor Input Select			MAX 187 AtoD		Switched Load	NC	NC

Status Register

Bit 5 of the Status Register is connected to Dout of the Max 187 AtoD.

MAX 187 12bit Serial AtoD Converter Pin out

1	VDD	Supply voltage, +5V \pm 5%
2	Ain	Sampling analogue input, 0V to VREF range
3	SHDN	Pulling SHDN high enables the internal reference
4	REF	Reference voltage - Sets analogue voltage range to 4.096V.
5	GND	Digital ground
6	Dout	DOUT Serial data output. Data changes state at SCLK's falling edge.
7	CS	Active-low Chip Select initiates conversions on the falling edge. When CS is high, DOUT is high impedance.
8	SCLK	Serial clock input. Clocks data out with rates up to 5MHz.


DG508 Multiplexer Pin out

1,15,16	A0, A1, A2	Address Inputs
2	EN	Enable. Take high to enable the IC
3, 13	V+, V-	Supply Voltage +/- 18V max
4,5,6,7,9,10,11,12	S1 to S7	Signal Input Lines
8	D	Switched Singal Output
14	GND	Ground (0v)

A 9 pin D type socket was selected for the battery analyser housing. A standard 25 pin D-type printer cable was used and a 9 pin D-type plug placed on the other end connected as below

25 pin D-type connected to PC Parallel Port		9 Pin D-type	Parallel Port Output / Input	Circuit Connection
Pin Number	Wire Colour	Pin Number		
2	Red	5	Data 0	Multiplexer A0
3	Orange	4	Data 1	Multiplexer A1
4	Pink	3	Data 2	Multiplexer A2
5	Yellow	2	Data 3	AtoD CS
6	Green	1	Data 4	AtoD SCLK
7	Light Blue	6	Data 5	Relay Control
11	White	7	Busy	AtoD Dout
25	Black/Grey	8	GND (0v)	GND (0v)

Software Screenshot

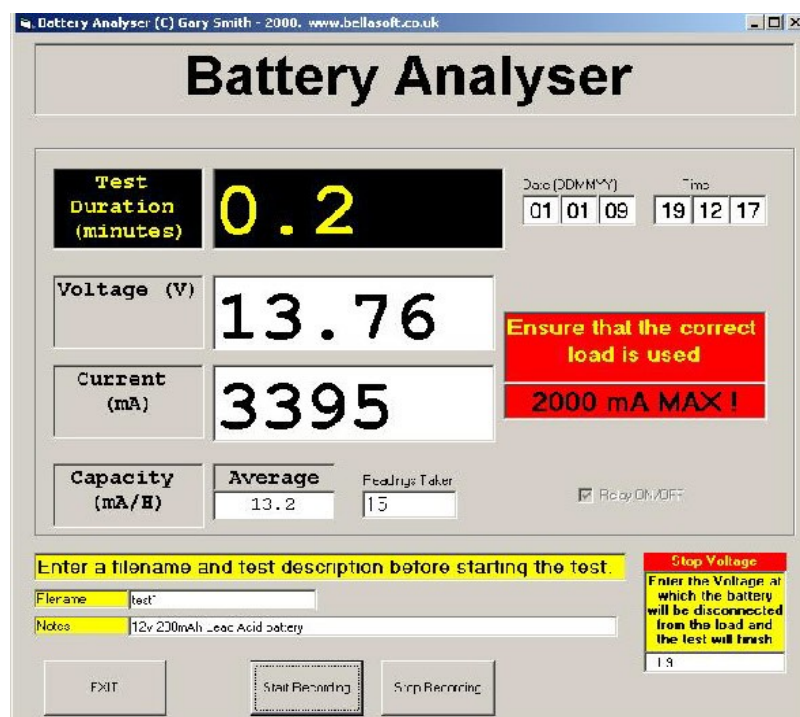

Visual Basic Project

Sensors.frm

Battery Analyser (C) Gary Smith - 2008. www.bellasoftware.co.uk

Battery Analyser

Test Duration (minutes) 00000

Voltage (V) 00000

Current (mA) 00000

Capacity (mA/H) 000

Average 000

Readings Taken 00000

Relay ON/OFF

Ensure that the correct load is used 2000 mA MAX !

Enter a filename and test description before starting the test.

Filename

Notes

EXIT Start Recording Stop Recording

Stop Voltage Enter the Voltage at which the battery will be disconnected from the load and the test will finish

Program Modules

InpOut32_Declarations

'Inp and Out declarations for port I/O using inpout32.dll.

```
Public Declare Function Inp Lib "inpout32.dll" Alias "Inp32" _
    (ByVal PortAddress As Integer) _
    As Integer
```

```
Public Declare Sub Out Lib "inpout32.dll" Alias "Out32" _
    (ByVal PortAddress As Integer, _
    ByVal Value As Integer)
```

```
Function BitStatus(PortNum%, BitYouWant%) As Integer
    NumOfBits% = 8
    ReDim PortBits(NumOfBits%) As Integer
    For i = 1 To NumOfBits%
        PortBits(i) = PortNum% Mod 2
        PortNum% = Fix(PortNum% / 2)
    Next i
    BitStatus = PortBits(BitYouWant%)
End Function
```

```
Function user_delay(delay) As Integer
    Dim n As Single
    n = Timer
    While Timer - n < delay: Wend
End Function
```

```

Function get_data(input_select, atod_output) As Integer
    Dim status_total As Integer
    Dim PortAddress As Integer
    'Change PortAddress to match the port address to write to:
    '(Usual parallel-port addresses are &h378, &h278, &h3BC)
    PortAddress = &H378
    ' put tick in relay on/off box
    sensors.relay.Value = 1
    atod_output = 0
    Out PortAddress, 32 + 8 + input_select 'CS High  SCLK Low -
    Out PortAddress, 32 + 0 + input_select 'CS Low   SCLK Low - Start a conversion
    ' Get bit of data
    For n = 11 To 0 Step -1
        ' Clock SCLK - Get bit of data
        Out PortAddress, 32 + 16 + input_select 'CS Low  SCLK High
        Out PortAddress, 32 + 0 + input_select 'CS Low  SCLK Low
        ' Read Status Port
        status_total = Inp(PortAddress + 1)
        status_total = 255 - status_total
        ' Get status of b7 (status port) - 1 or 0.
        status_total = BitStatus(status_total, 8)
        If status_total = 1 Then atod_output = atod_output + (2 ^ n)
    Next n
    DoEvents
End Function

Function select_input_channel(input_select) As Integer
    ' First select input channel
    Out PortAddress, input_select
    ' Small delay while Multiplexor switches input channels
    Call user_delay(0.2)
End Function

Function toggle_relay() As Integer
    Dim PortAddress As Integer
    PortAddress = &H378
    If sensors.relay.Value = 1 Then Out PortAddress, 32
    If sensors.relay.Value = 0 Then Out PortAddress, 0
End Function

Function relay_off() As Integer
    Dim PortAddress As Integer
    PortAddress = &H378
    Out PortAddress, 0
End Function

```


sensors.frm Program Modules

```
Option Explicit
Dim Value As Integer
Dim input_select As Integer
Dim atod_output As Integer
Dim atod_voltage As Single
Dim atod_current As Integer
Dim atod_avg As Long
Dim monitor_flag As Boolean
Dim elapsed As Long
Dim avg_current As Single
Dim max_current As Single
Dim total_current As Single
Dim readings As Long

Private Sub button_exit_Click()
    ' Turn off relay before exiting program
    sensors.relay.Value = 0
    Call toggle_relay
End
End Sub

Private Sub button_start_recording_Click()
Dim lop As Integer
Dim response
relay.Enabled = False
monitor_flag = True
If Text_vstop.Text = "" Then
    response = MsgBox("You need to enter the voltage at which the battery will be disconnected.
    Failure to do this will result in the battery being discharged to 0 Volts. Enter a value in the
    Stop Voltage box. You can enter this value during the test. ", vbOKOnly, "WARNING")
End If
elapsed = 0
avg_current = 0
max_current = 0
total_current = 0
readings = 0

Open Text_filename.Text + ".txt" For Append As #1
Print #1, Text_description.Text
Close #1

While (monitor_flag = True)
    DoEvents
    Rem *****
    Rem ***** input select : 0=voltage, 1=current *****
    Rem *****
    For input_select = 0 To 1
        ' Take a reading
        ' Select voltage or current input to multiplexer
```

```

    Call select_input_channel(input_select)

' Get Average of 100 readings
atod_avg = 0
For lop = 1 To 1000
' Get AtoD output
    Call get_data(input_select, atod_output)
    atod_avg = atod_avg + atod_output
Next lop
atod_output = atod_avg / 1000

' Display AtoD Output Voltage
If input_select = 0 Then
    atod_voltage = atod_output / 297.5
    ' Set number of decimal places depending on battery voltage
    If atod_voltage > 10 Then atod_voltage = Round(atod_voltage, 2) Else atod_voltage = Round(atod_voltage, 3)
    text_atod_output(input_select).Text = atod_voltage
End If
If atod_voltage < Val(Text_vstop.Text) And elapsed > 5 Then monitor_flag = False
' Current
If input_select = 1 Then
    atod_current = atod_output / 1.203
    atod_current = atod_current - 9
    text_atod_output(input_select).Text = atod_current
    total_current = total_current + atod_current
    readings = readings + 1
    avg_current = total_current / readings
    Text_avg.Text = Round(avg_current * (elapsed / 3600), 1)
    Text_readings.Text = readings
End If
Next input_select

' Add test results to the file
Open Text_filename.Text + ".txt" For Append As #1
Print #1, Label_elapsed_m, text_atod_output(0).Text, text_atod_output(1).Text
Close #1
Label_elapsed_m.Caption = Round(elapsed / 60, 1)
Wend

' Turn off lamp
Call relay_off
relay.Value = False
response = MsgBox("The test has finished", vbOKOnly, "Finished")
relay.Enabled = True
Open Text_filename.Text + ".txt" For Append As #1
Print #1, "*****"
Print #1, "*** BATTERY CAPACITY (mAh)"
Print #1, "***"
Print #1, "*** "; Text_avg.Text
Print #1, "***"

```

```

Print #1, "*****"
Close #1
End Sub

Private Sub button_stop_recording_Click()
    monitor_flag = False
End Sub

Private Sub relay_Click()
    Call toggle_relay
End Sub

Private Sub Timer1_Timer()
    ' Only enable the start button once a filename and description have been entered
    elapsed = elapsed + 1
    If Text_filename.Text <> "" And Text_description.Text <> "" Then
        button_start_recording.Enabled = True
    Else: button_start_recording.Enabled = False
    End If
    ' Display the date and time
    Text_seconds = Mid$(Time, 7, 2)
    Text_mins = Mid$(Time, 4, 2)
    Text_hours = Mid$(Time, 1, 2)
    Text_day = Mid$(Date, 1, 2)
    Text_month = Mid$(Date, 4, 2)
    Text_year = Mid$(Date, 9, 2)
    If Label12.ForeColor = vbYellow Then Label12.ForeColor = vbBlack Else Label12.ForeColor = vbYellow
End Sub

Private Sub y_Click()
    Call relay_off
End
End Sub

```